ChipName: Mux 8 Way 16
Inputs: a[16], b[16], ...g[16], h[16], sel[3]
Outputs: out[16] Function: aut = a if sel = 000 b if sel = 001 h if sel = 111 sel[2] Selo] sel[1]