CHIP Name: MUX16

Tapols: a[16], b[16], sel

Outpols: out[16]

Function: if sel = 0 then for i=0...15 out(i) = a(i)
else for i=0...15 out(i) = b(i)

