
Chip Name: Bit (Binary Cell)

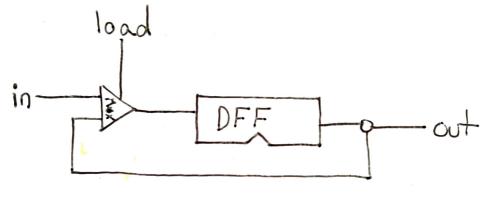Inputs: in, load Outputs: out Function: if load (+-1) then out(+)=in(+-1)else out(+)=out(+-1)



Note, function of DFF: out (+) = in (+-1)