

Chip Name: Half Adder

Inputs: a, b

Outputs: sum (LSB of $a+b$)

Function: carry (MSB of $a+b$)

Inputs			
a	b	carry	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

